


Name:  
Surname:

EE 208\_Lab\_Quiz 2

18.05.2017


Question:

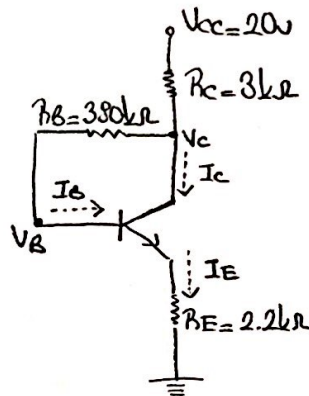a) Construct below collector feedback configuration;



b) Assume that  $\beta = 300$ . Calculate the values of  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_B$ ,  $V_C$  and  $V_{CE}$ .

Transistor is 2N3804

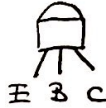

- Solution -

$$V_C = V_{CC} - R_C \cdot (I_C + I_B) \Rightarrow V_C = 20 - (3 \cdot 10^3)(\beta + 1)I_B \Rightarrow V_C = 20 - (3000)(301)I_B = 20 - 900000I_B \Rightarrow$$

$$V_E = V_B - V_{BE} = I_E R_E \Rightarrow V_E = (\beta + 1)I_B (2.2) \cdot 10^3 \Rightarrow \boxed{V_E \approx 6.54V}$$

$$\boxed{V_C \approx 11.108V}$$

$$V_{CE} = V_C - V_E = 11.108 - 6.54 \Rightarrow \boxed{V_{CE} \approx 4.568V}$$

$$V_B = V_{BE} + V_E \Rightarrow V_B = 0.7 + (301)(2.2) \cdot 10^3 I_B \Rightarrow \boxed{V_B \approx 7.242V}$$

$$I_B = \frac{V_C - V_B}{R_B} \Rightarrow I_B = \frac{(20 - 900000I_B) - (0.7 + (301)(2.2) \cdot 10^3 I_B)}{(380) \cdot 10^3} = \frac{19.3 - 900000I_B - 662200I_B}{380000} = \frac{19.3 - 1562200I_B}{380000} \Rightarrow \boxed{I_B \approx 9.88\mu A}$$

$$I_E = I_C + I_B \Rightarrow \boxed{I_E \approx I_C \approx 2.964\text{ mA}}$$

$$I_C = \beta \cdot I_B \Rightarrow \boxed{I_C \approx 2.964\text{ mA}}$$


Name:  
Surname:

EE 208\_Lab. Q12.2

18.05.2017


Question:

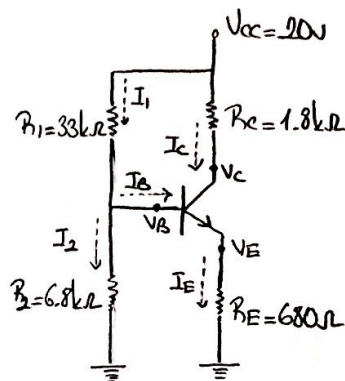a) Construct below voltage divider configuration;



b) Assume that  $\beta = 300$ . Calculate the values of  $I_B, I_C, I_E, V_B, V_C$  and  $V_{CE}$ .

Transistor is 2N3904

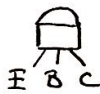

- Solution -

$$V_C = V_{CC} - R_C \cdot I_C \Rightarrow V_C = 20 - (1.8) \cdot 10^3 \cdot I_C \Rightarrow V_C = 20 - (1.8 \times 10^3) (4.53) (10^{-6}) \Rightarrow \boxed{V_C \approx 18.99V}$$

$$V_E = I_E \cdot R_E = V_B - V_{BE} \Rightarrow V_E = 3.417 - 0.7 \Rightarrow \boxed{V_E \approx 2.717V}$$

$$V_{CE} = V_C - V_E = 18.99V - 2.717V \Rightarrow \boxed{V_{CE} \approx 17.273V}$$

$$V_B = V_{BE} + V_E = V_{CC} \left( \frac{R_2}{R_1 + R_2} \right) \rightarrow (\text{voltage divider}) \Rightarrow V_B = 20 \cdot \left( \frac{(6.8) \cdot 10^3}{(33) \cdot 10^3 + (6.8) \cdot 10^3} \right) \Rightarrow \boxed{V_B \approx 3.417V}$$

$$I_2 = \frac{V_B}{R_2} \Rightarrow I_2 = \frac{3.417V}{(6.8) \cdot 10^3} \Rightarrow \boxed{I_2 \approx 0.5mA}$$

$$I_1 = I_2 + I_B = \frac{V_{CC} - V_B}{R_1} \Rightarrow I_1 = \frac{20 - 3.417}{(33) \cdot 10^3} \Rightarrow \boxed{I_1 \approx 0.502mA} \Rightarrow I_B = I_1 - I_2 \Rightarrow \boxed{I_B \approx 0.0151mA}$$

$$I_C = \beta \cdot I_B = (300)(0.0151mA) \Rightarrow \boxed{I_C \approx 4.53\mu A}$$

$$I_E = I_C + I_B \Rightarrow \boxed{I_E \approx 4.54\mu A \approx I_C}$$