
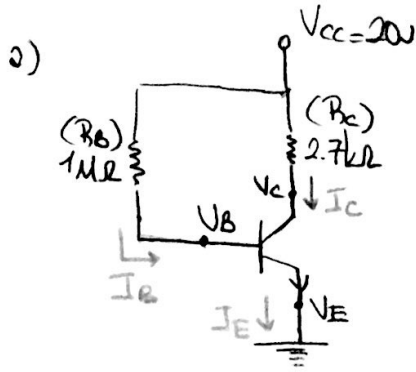


## Part 1

\* Use 2N3904 



b) Measure the voltages  $V_{BE}$  and  $V_{CE}$ .

c) 
$$I_B = \frac{20 - V_{BE}}{1M\Omega}, \quad I_C = \frac{V_{CE}}{2.7k\Omega}$$

\* Since  $R_B$  resistance value is so high, there will be a multimeter loading effect.

In order to avoid the loading effect, we should measure  $V_{BE}$  instead of measuring the voltage on  $R_B$  directly.

d) Insert your values in Table 8.1. Find  $\beta$  value.  $\beta = I_C / I_B$

## Part 2

a) Again find  $I_B$  and  $I_C$  values by calculation; compare them with the measured values.

$$I_B = \frac{20 - 0.7}{1M\Omega} = 19.3\mu A$$

$$I_C = \beta \cdot I_B$$

b) Calculate  $V_B$ ,  $V_C$ ,  $V_E$  and  $V_{CE}$ :

$$V_B = 20 - I_B(1M\Omega)$$

$$V_C = 20 - I_C(2.7k\Omega)$$

$$V_E = 0$$

c) Measure  $V_B$ ,  $V_C$ ,  $V_E$  and  $V_{CE}$  from the circuit. Insert  $V_{CE}$  value in Table 8.1.

d) Remove 2N3904, and insert 2N4401 transistor. Repeat same steps for this case as well. Record your values in Table 8.1, find  $\beta$  for this transistor.

e) Calculate the magnitude of the percent change in each quantity due to a change in transistors.